

(13.18) a) relation 13.9: $i(t) = \frac{U}{R} e^{-\frac{1}{\tau}t}$ (courant de charge)

On part de $u(t) = U(1 - e^{-\frac{1}{\tau}t})$

$$\text{Sachant que } i(t) = C \frac{d}{dt} u(t) = C \frac{d}{dt} \left(U(1 - e^{-\frac{1}{\tau}t}) \right) = CU \frac{d}{dt} (1 - e^{-\frac{1}{\tau}t}) = CU \frac{1}{\tau} e^{-\frac{1}{\tau}t}$$


$$= CU \frac{1}{RC} e^{-\frac{1}{\tau}t} = \frac{U}{R} e^{-\frac{1}{\tau}t}$$

b) relation 13.11: $i(t) = \frac{U}{R} e^{-\frac{1}{\tau}t}$ (courant de décharge)

On part de $u(t) = U e^{-\frac{1}{\tau}t}$

$$\text{Comme } i(t) = C \frac{d}{dt} u(t) = CU \frac{d}{dt} e^{-\frac{1}{\tau}t} = CU \left(-\frac{1}{\tau} \right) e^{-\frac{1}{\tau}t} = \underline{\underline{-\frac{U}{R} e^{-\frac{1}{\tau}t}}}$$

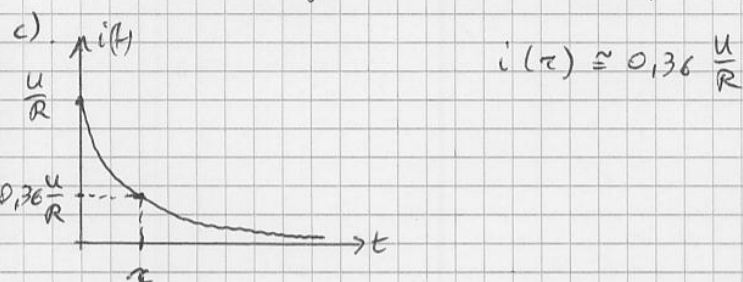le courant de décharge a une direction opposée au courant de charge.



(13.21) a) relation à démontrer: $u(t) = U e^{-\frac{1}{\tau}t}$ $\tau = \frac{L}{R}$

On part de la relation 13.12: $i(t) = \frac{U}{R} (1 - e^{-\frac{1}{\tau}t})$

Pour le charge de l'inductance, on a $u(t) = L \frac{di}{dt}$

$$\Rightarrow \frac{di}{dt} = -\frac{U}{R} \cdot \left(-\frac{1}{\tau} \right) e^{-\frac{1}{\tau}t}$$

$$\Rightarrow u(t) = L \frac{U}{R} \cdot \frac{R}{L} e^{-\frac{1}{\tau}t} = \underline{\underline{U e^{-\frac{1}{\tau}t}}}$$

b) relation à démontrer: $u(t) = U e^{-\frac{1}{\tau}t}$

On part de la relation 13.14: $i(t) = \frac{U}{R} e^{-\frac{1}{\tau}t}$

$$\Rightarrow \frac{di}{dt} = -\frac{R}{L} \frac{U}{R} e^{-\frac{1}{\tau}t} = -\frac{U}{L} e^{-\frac{1}{\tau}t}$$

$$\Rightarrow u(t) = L \frac{di}{dt} = \underline{\underline{-U e^{-\frac{1}{\tau}t}}}$$

lors de la décharge,
la tension est opposée
à la tension lors de la
charge

