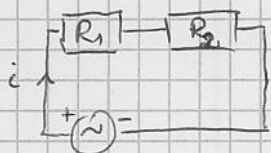


13.42 $U_{eff} = 12V$; $R_1 = R_2 = 47\Omega$


a) $f \rightarrow \infty$



$\therefore f \rightarrow \infty, Z_C \rightarrow 0$ et $Z_L \rightarrow \infty$
 $\downarrow$ $\downarrow$
 circuit fermé circuit ouvert

$$\Rightarrow I_{eff} = \frac{U_{eff}}{R_{Tda}} = \frac{12V}{94\Omega} \approx \underline{0,128A}$$

b) $f \rightarrow 0$

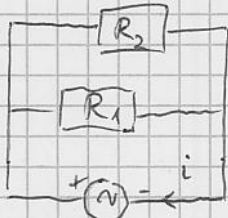


$\therefore f \rightarrow 0, Z_C \rightarrow \infty$ et $Z_L \rightarrow 0$
 $\downarrow$ $\downarrow$
 circuit ouvert circuit fermé

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{47} + \frac{1}{47} = \frac{2}{47} \quad \Rightarrow R_{eq} = \frac{47}{2} = 23,5\Omega$$


$$\Rightarrow I_{eff} = \frac{U_{eff}}{R_{eq}} = \frac{12V}{23,5\Omega} \approx \underline{0,51A}$$

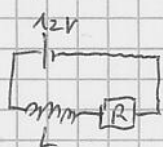13.43 • tension constante L n'a aucun effet! $\Rightarrow$ permet de déterminer R



$$\hat{I} = \frac{U_{eff}}{R} \sqrt{2} \Rightarrow R = \frac{U_{eff}}{\hat{I}} = \frac{12}{I_{eff}} \quad (1)$$

• tension variable

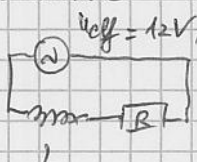

$$Z = \frac{\hat{U}}{\frac{1}{\sqrt{2}} \hat{I}} = \frac{U_{eff}}{\frac{1}{\sqrt{2}} I_{eff}} = \sqrt{R^2 + (2\pi f L)^2} = \frac{36}{I_{eff}} \quad (2)$$

$$\text{de (1)} : I_{eff} = \frac{12}{R} \Rightarrow \text{dans (2)} : \sqrt{R^2 + (2\pi \cdot 4,2)^2} = \frac{36R}{12} = 3R$$

$$\Rightarrow R^2 + (8,4\pi)^2 = 9R^2$$

$$\Rightarrow 8R^2 = (8,4\pi)^2$$

$$\Rightarrow R = \sqrt{\frac{(8,4\pi)^2}{8}} \approx \underline{9,3\Omega}$$

13.44 • fréquence $Z_C \rightarrow \infty$: $Z = \frac{\hat{U}}{\hat{I}_0} = R = 16 \Rightarrow \hat{I}_0 = \frac{\hat{U}}{16}$

$$\text{• fréquence } f : Z_f = \frac{\hat{U}}{\hat{I}_f} = \sqrt{R^2 + (2\pi f L)^2} = \frac{\hat{U}}{\frac{1}{2} \hat{I}_0} = 2 \cdot \frac{\hat{U}}{\hat{I}_0} = 32$$

$$\Rightarrow R^2 + (2\pi f L)^2 = 32^2$$

$$16^2 + \left(2\pi f \frac{4}{1000}\right)^2 = 32^2 \Rightarrow \left(2\pi f \frac{4}{1000}\right)^2 = 32^2 - 16^2 \Rightarrow f = \frac{\sqrt{32^2 - 16^2}}{2\pi \cdot \frac{4}{1000}} \approx \underline{1103\text{Hz}}$$