

13.65


$$u_{eff} = 26,0V$$

$$I_{eff} = 0,141A$$

$$R = 108\Omega$$

$$C = 2,00 \cdot 10^{-7}F$$

$$L = 5,42 \cdot 10^{-3}H$$

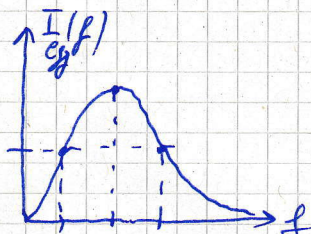

$$I_{eff} = \frac{u_{eff}}{Z} = u_{eff} \cdot \left[ R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 \right]^{-1/2}$$

$$\sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2} = \frac{u_{eff}}{I_{eff}} = Z$$

on élève au carré

$$\omega L < \frac{1}{\omega C} \quad \omega L = \frac{1}{\omega C} \quad \omega L > \frac{1}{\omega C}$$

$$R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 = Z^2$$

$$\downarrow -R^2$$

$$\left( \omega L - \frac{1}{\omega C} \right)^2 = Z^2 - R^2$$

$$\omega L - \frac{1}{\omega C} = \pm \sqrt{Z^2 - R^2} \quad ("+" = f_2 // "-" = f_1)$$

$$\downarrow \cdot \omega$$

$$\omega^2 L - \frac{1}{C} = \pm \sqrt{Z^2 - R^2} \omega$$

forme canonique

$$\omega^2 L \pm \sqrt{Z^2 - R^2} \omega - \frac{1}{C} = 0$$

$$\downarrow \div L$$

$$\omega^2 \pm \frac{\sqrt{Z^2 - R^2}}{L} \omega - \frac{1}{LC} = 0$$

$$\omega_{1,2} = \frac{\pm \sqrt{Z^2 - R^2}/L \pm \sqrt{\left( \frac{Z^2 - R^2}{L^2} + \frac{4}{LC} \right)}}{2}$$

|     |                                 |  |
|-----|---------------------------------|--|
| ++  | $4,71 \cdot 10^4 \frac{rad}{s}$ |  |
| + - | < 0                             |  |
| - + | $1,96 \cdot 10^4 \frac{rad}{s}$ |  |
| --  | < 0                             |  |

$$Z^2 - R^2 = (A)$$

$$\sqrt{A} = (B)$$

$$\frac{\sqrt{Z^2 - R^2}}{L} = (C)$$

Les 2 réponses possibles sont :

$$f_1 = 3,11 \cdot 10^3 Hz \hat{=} 1,96 \cdot 10^4 \frac{rad}{s}$$

$$f_2 = 7,50 \cdot 10^3 Hz \hat{=} 4,71 \cdot 10^4 \frac{rad}{s}$$